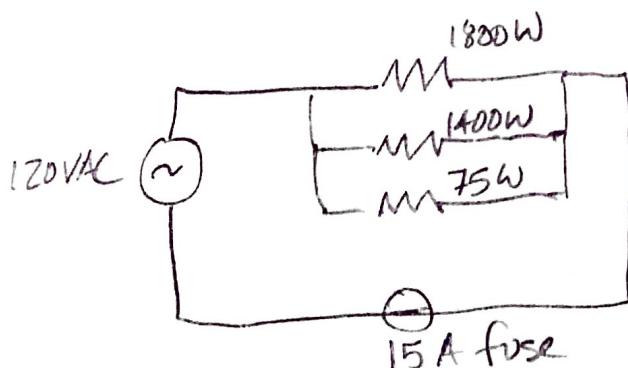


10.28

Devices are connected in parallel:



a) Current drawn by each device?

$$P = IV \rightarrow 1800W = I(120V)$$


$$I = \frac{1800}{120} = \boxed{15A} \text{ toaster.}$$

$$I_{\text{speaker}} = \frac{1400W}{120} = \boxed{11.7A}$$

$$I_{\text{lamp}} = \frac{75}{120} = \boxed{0.625A}$$

b) The speaker & the lamp together would need 12.3 A, & that's fine. But that toaster is 15 A all by itself. If in combination with anything else will cause too much current to flow, & the fuse/circuit breaker will blow.

10.25

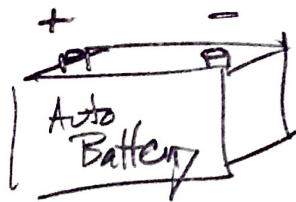

$V_{\text{terminal}} = 16.0 \text{ V}$ during charging

$$I = 10.0 \text{ A}$$

$\mathcal{E}$ for battery is 12.0 V , so

$$\begin{aligned} \text{a) } V_{\text{terminal}} &= \mathcal{E} - Ir \\ 16 \text{ V} &= 12 - (10 \text{ A})r \end{aligned}$$

When battery is being charged current flows in the opposite direction that it is delivered,

so

$$16 \text{ V} = 12 - (-10)r$$

$$\frac{16 - 12}{10} = r = \boxed{0.40 \Omega}$$

$$\begin{aligned} \text{b) Power dissipated (using resistance)} \\ = I^2 R = (10 \text{ A})^2 (0.40 \Omega) = \boxed{40 \text{ W}} \end{aligned}$$

c) At what rate will temperature increase $^{\circ}\text{C}/\text{min}$?

$m = 20.0 \text{ kg}$ & specific heat $C = 0.300 \text{ kcal/kg}^{\circ}\text{C}$?

$$Q = mC\Delta T ! \text{ :)$$

$$P = \frac{Q}{t}, \text{ so } P = \frac{mC\Delta T}{t}$$


$$40 \frac{\text{J}}{\text{s}} = (20 \text{ kg}) (0.300 \frac{\text{kcal}}{\text{kg}^{\circ}\text{C}}) \frac{\Delta T}{t}$$

$$\frac{1 \text{ kcal}}{4.184 \text{ J}} \times 40 \frac{\text{J}}{\text{s}} = 6000 \frac{\text{cal}}{\text{s}} \frac{\Delta T}{t} \times \frac{1 \text{ min}}{60 \text{ s}}$$

$$\frac{\Delta T}{s} = \frac{40}{4.184 \times 6000} = 0.00159 \frac{^{\circ}\text{C}}{\text{s}} \times \frac{60 \text{ s}}{\text{min}} =$$

$$\boxed{9.56 \times 10^{-2} ^{\circ}\text{C}/\text{min}}$$


10.26

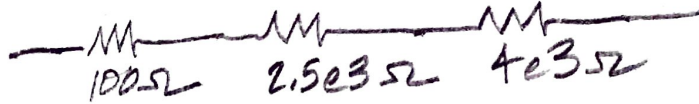

a) In series, $R_{\text{equivalent}} = R_1 + R_2 + R_3$

$$= \begin{array}{r} 100 \\ 2500 \\ 4000 \\ \hline 6600 \end{array} \Omega$$

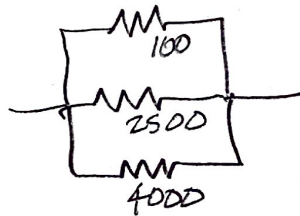b) In parallel, $\frac{1}{R_{\text{equivalent}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$



$$R_{\text{equivalent}} = 93.9 \Omega$$