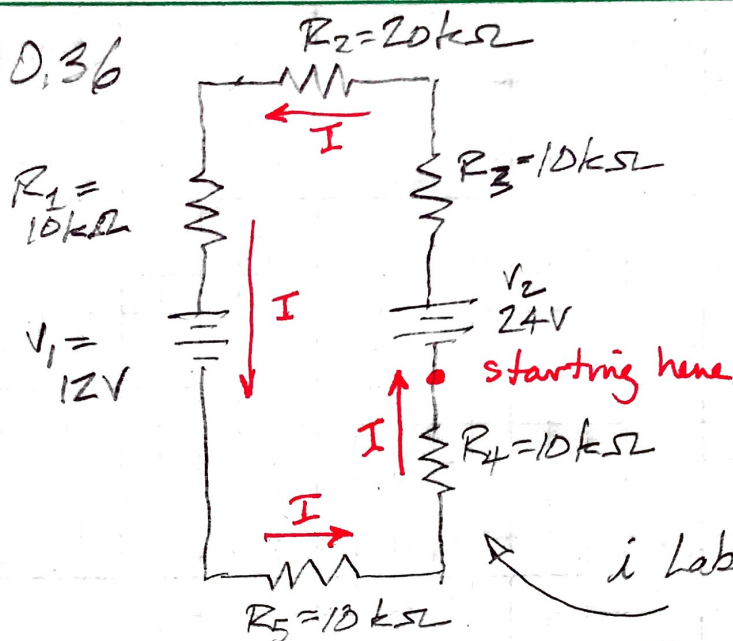


10.36



a) Find voltage across each resistor. To do these, we need to find current, which is relatively easy, given that there's just one loop & no junctions. i Label current & guess direction ✓

ii Trace through circuit:

$$+24 - \underset{R_3}{10000I} - \underset{R_2}{20000I} - \underset{R_1}{10000I} - 12 - \underset{R_4}{10000I} - \underset{R_5}{10000I} = 0$$

Simplify: $12V - 60000I = 0$
 $12 = 60000I$
 $I = \frac{12}{60000} = 2.0 \times 10^{-4} A = 0.20 \text{ mA}$

Oh, but they want the Voltage across each resistor:

$$\begin{aligned} V_1 &= IR_1 = (2 \times 10^{-4})(10000) = 2.0 \text{ Volts} \\ V_2 &= IR_2 = (2 \times 10^{-4})(20000) = 4.0 \text{ Volts} \\ V_3 &= 2.0V \\ V_4 &= 2.0V \\ V_5 &= 2.0V \end{aligned}$$

b: Power dissipated & Power supplied?

$$P_{\text{supplied}} = IV = (2 \times 10^{-4} A)(24V) = 4.8 \times 10^{-3} \text{ Watts}$$

$$P_{\text{dissipated}} = IV \text{ for each resistor, or } \frac{I^2 R, \text{ or } \frac{V^2}{R}$$

$$P_1 = I^2 R_1 = (0.0002)^2 (10000) = 4 \times 10^{-4} \text{ W}$$

$$P_2 = 8 \times 10^{-4} \text{ W}$$

$$P_3 = 4 \times 10^{-4} \text{ W}$$

$$P_4 = 4 \times 10^{-4} \text{ W}$$


$$P_5 = 4 \times 10^{-4} \text{ W}$$

If you add these up we're only dissipating half the

Power supplied by the 24V battery.

The other battery, 12V, w/ current running "backwards" through it, is dissipating $P = -IV = 2.4 \times 10^{-3} \text{ W}$.

10.37

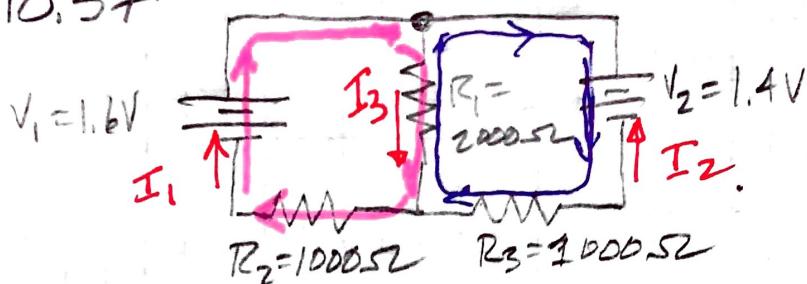

a) Find current through each resistor.

1. Identify current branches, labels, & directions.
2. Use node (junction) rule to get an equation.

$$\sum I_{in} = \sum I_{out}$$

$$I_1 + I_2 = I_3$$

No more junction eqns will help, so additional equations (total of 3 eqns to solve the 3 unknowns) must be loop rule equations.

3. Use loop rule to get eqns.

Clockwise around left loop.

$$1.6V - 2000I_3 - 1000I_1 = 0$$

Clockwise around right loop.

$$-1.4V + 1000I_2 + 2000I_3 = 0$$

4. Use 3 simultaneous eqns & solve, by hand or w/ calculator:

$$\left. \begin{array}{l} \frac{1}{1000}I_1 + \frac{1}{2000}I_2 - \frac{1}{2000}I_3 = 0 \\ 1000I_1 + 0I_2 + 2000I_3 = 1.6 \\ 0I_1 + 1000I_2 + 2000I_3 = 1.4 \end{array} \right\} \text{Solving}$$

$$\boxed{I_1 = 4.0e-4A, I_2 = 2.0e-4A, I_3 = 6.0e-4A}$$

c) Power dissipated by each circuit = power produced.


Either added up all the $P = I^2R$ values, or add up the $P = IV$ for the batteries. (easier!)

$$P_{total} = I_1V_1 + I_2V_2$$

$$= (4.0e-4A)(1.6V) + (2.0e-4A)(1.4V)$$

$$= \boxed{9.2e-4 \text{ Watts}}$$

10.38

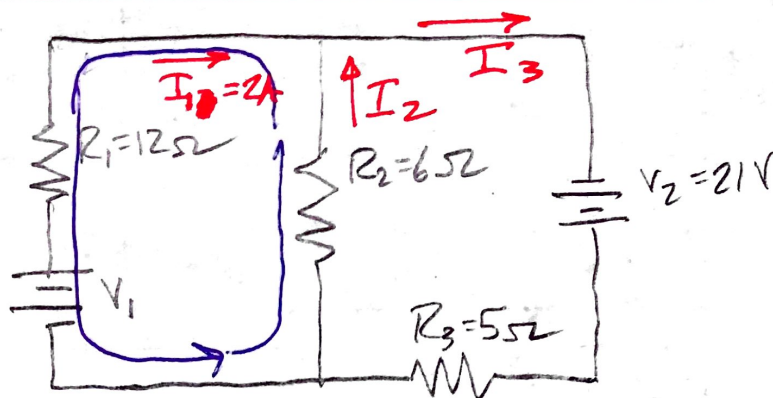

Solve using same strategy:

Junction Rule: $I_1 + I_2 = I_3$
 $2 + I_2 = I_3$
 $0I_1 + 1I_2 - 1I_3 = -2$ ✓

Loop Rule:
 Left loop (counterclockwise)
 $-6I_2 + 12I_1 - V_1 = 0$
 $12I_1 - 6I_2 + 0I_3 = V_1$ ✓

Right loop (clockwise)
 $21V - 5I_3 - 6I_2 = 0$
 $0I_1 - 6I_2 - 5I_3 = -21$ ✓

$$\left[\begin{array}{ccc|c} 0 & 1 & -1 & -2 \\ 12 & -6 & 0 & V_1 \\ 0 & -6 & -5 & -21 \end{array} \right]$$

$$I_1 = 2.0 \text{ (given)}$$

$$I_2 = +1.0$$

$$I_3 = 3.0 \text{ A}$$

$$V_1 = 18 \text{ V}$$

Can't resolve these symbolically in calculator, so solve by hand w/ matrix